

Electronic Quiz Buzzer Circuit using FSM

MINI PROJECT

Abstract-

Quiz competitions are held in various special programs, the process of identifying the candidate who pressed the button is very critical in timing and might differ in milliseconds.

This process is made simpler using this electronic quiz buzzer circuit. The indicator corresponding to the candidate (assume there are three candidates) should be active (led and buzzer on) who has pressed the switch first. After the indication from first switch being pressed (even if pressed momentarily), pressing of another switch does not give any indication. The system is reset for next round when instructor presses the reset/clear button.

The circuit is made using AND gate, OR gate ICs, and a couple of SR type Flipflop, hence the circuit is cost effective.




Fastest Finger First

Electronic Quiz Buzzer Circuit

Methodology-

1. The switches for candidates A,B,C are x_2, x_1, x_0 (input) respectively
2. Output is Z_2, Z_1, Z_0
3. If candidate A presses switch first input sequence is 001, state reached is 01 switching on first led only, producing output as $z_2=0, z_1=0, z_0=1$. If after this another switch is pressed(high) the output remains unaffected until clear is applied.
4. If candidate B presses switch first input sequence is 010, state reached is 10 switching on first led only. If after this another switch is pressed(high) the output remains unaffected until clear is applied.
5. If candidate C presses switch first input sequence is 100, state reached is 11 switching on first led only. If after this another switch is pressed(high) the output remains unaffected until clear is applied.

State Diagram

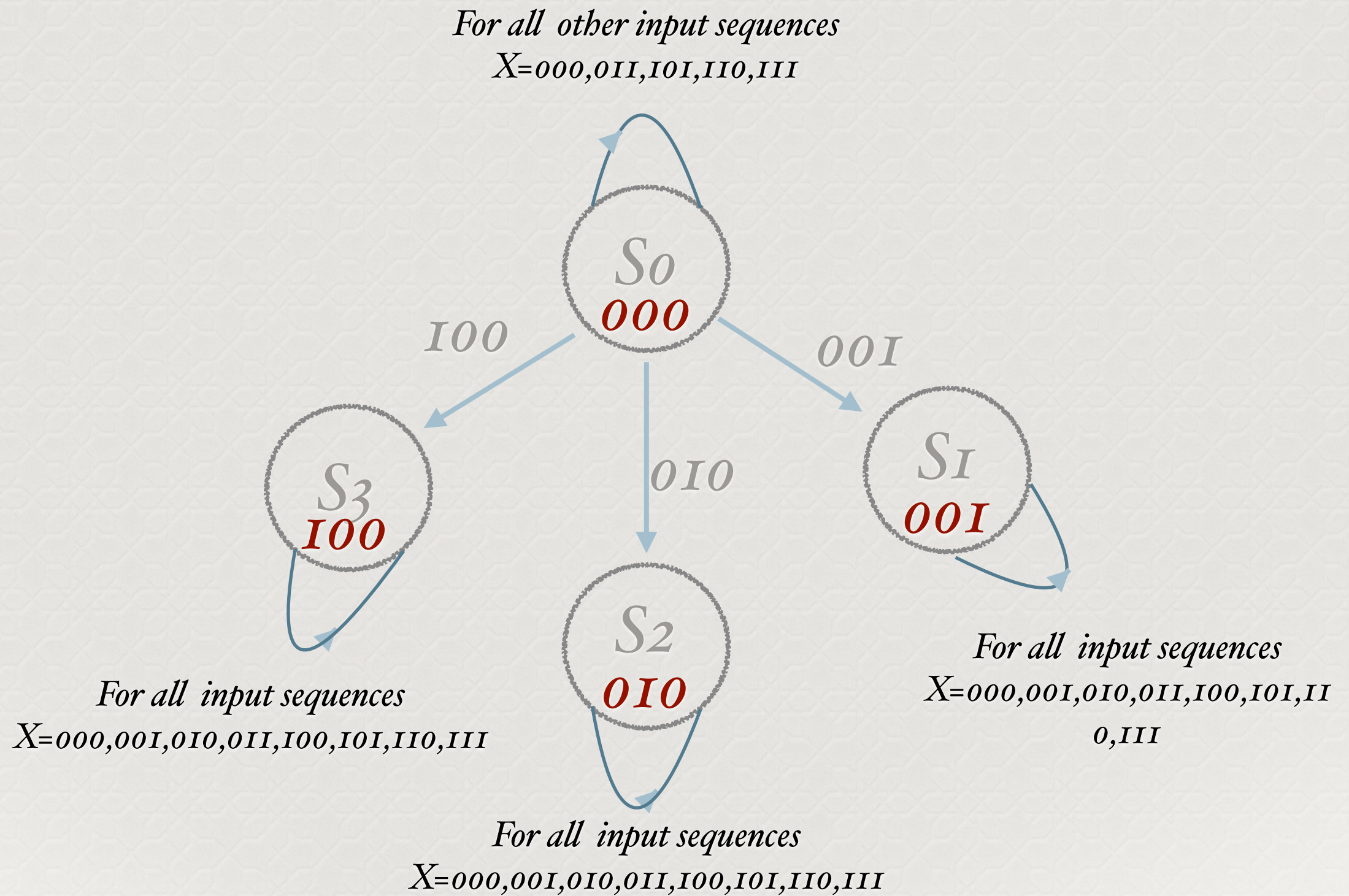

State Table:

[illegible]

1. Circuit is implemented using D flip flops

2 The number of flipflop = shortest integer function ($\log_2(\text{no. of states})$)
 $= \text{SIF}(\log_2(4)) = 2$

3 Using Shannons decomposition theorem D_0, D_1 are evaluated for each case of present state (PS) individually

I.e. $D_i = Q'_1 Q'_0 (F_1(D_i)) + Q'_1 Q_0 (F_2(D_i)) + Q_1 Q'_0 (F_3(D_i)) + Q_1 Q_0 (F_4(D_i))$

$PS(Q_n) = Q'_1 Q'_0$

Input	PS	NS	$D = Q_{n=1}$	
$x_2 x_1 x_0$	Q_n	Q_{n+1}	D_1	D_0
000	00	00	0	0
001	00	01	0	1
010	00	10	1	0
011	00	11	0	0
100	00	00	1	1
001	00	00	0	0
010	00	00	0	0
111	00	00	0	0

Kmap for PS(Qn)=Q'IQ'o

$\begin{array}{c} xIx0 \\ x2 \end{array}$	00	01	11	10
0	0	0	0	1
1	1	0	0	0

D_I

$$D_I = x'o(xIx'2 + x'Ix2)(Q'oQ'I)$$

$\begin{array}{c} xIx0 \\ x2 \end{array}$	00	01	11	10
0	0	1	0	0
1	1	0	0	0

D_o

$$D_o = x'I(x'o x2 + x0 x'2)(Q'oQ'I)$$

PS(Qn)=Q'IQo

Input(all)	PS	NS		
x2xIx0	Qn	Qn+1	D _I =0	D _o =1

D_I=0

D_o=(Q'IQo)

$$PS(Q_n)=Q_I Q'_o$$

Input(all)	PS	NS		
x2xIXO	Q _n	Q _{n+I}	D _{I=I}	D _{O=O}

$$D_{O=O}$$

$$D_I=(Q_I Q'_o)$$

$$PS(Q_n)=Q_I Q_o$$

Input(all)	PS	NS		
x2xIXO	Q _n	Q _{n+I}	D _{I=I}	D _{O=I}

$$D_{O=O}=(Q_I Q_o)$$

$$D_{O=O}=(Q_I Q_o)$$

Asynchronous clear input is used to clear states at any time by instructor, Combining all the cases and asynchronous clear final D_I, D_O

$$D_I = [Q_I Q'_O + Q_I Q_O + Q'_I Q'_O X'_O (X_I \text{ xor } X_2)] \text{Clr}$$

$$D_O = [Q'_I Q_O + Q_I Q_O + Q'_I Q'_O X'_I (X_O \text{ xor } X_2)] \text{Clr}$$

Output

$$Z_O = Q'_I Q_O$$


$$Z_I = Q_I Q'_O$$


$$Z_2 = Q_I Q_O$$

$$\text{Buzzer - on when one of the op is on} = Z_O + Z_I + Z_2$$


Electronic buzzer circuit using Logisim

Simulation snapshots

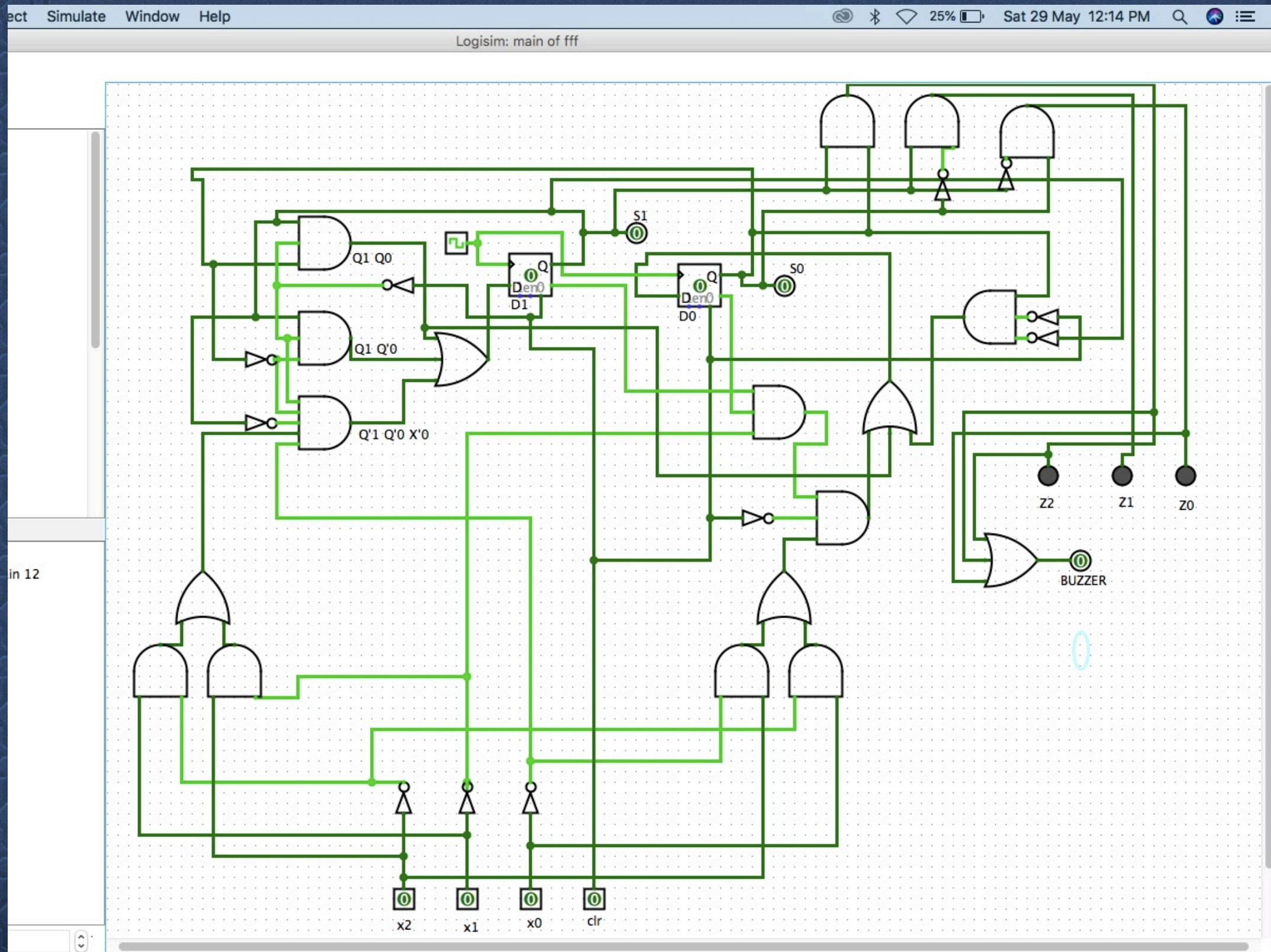


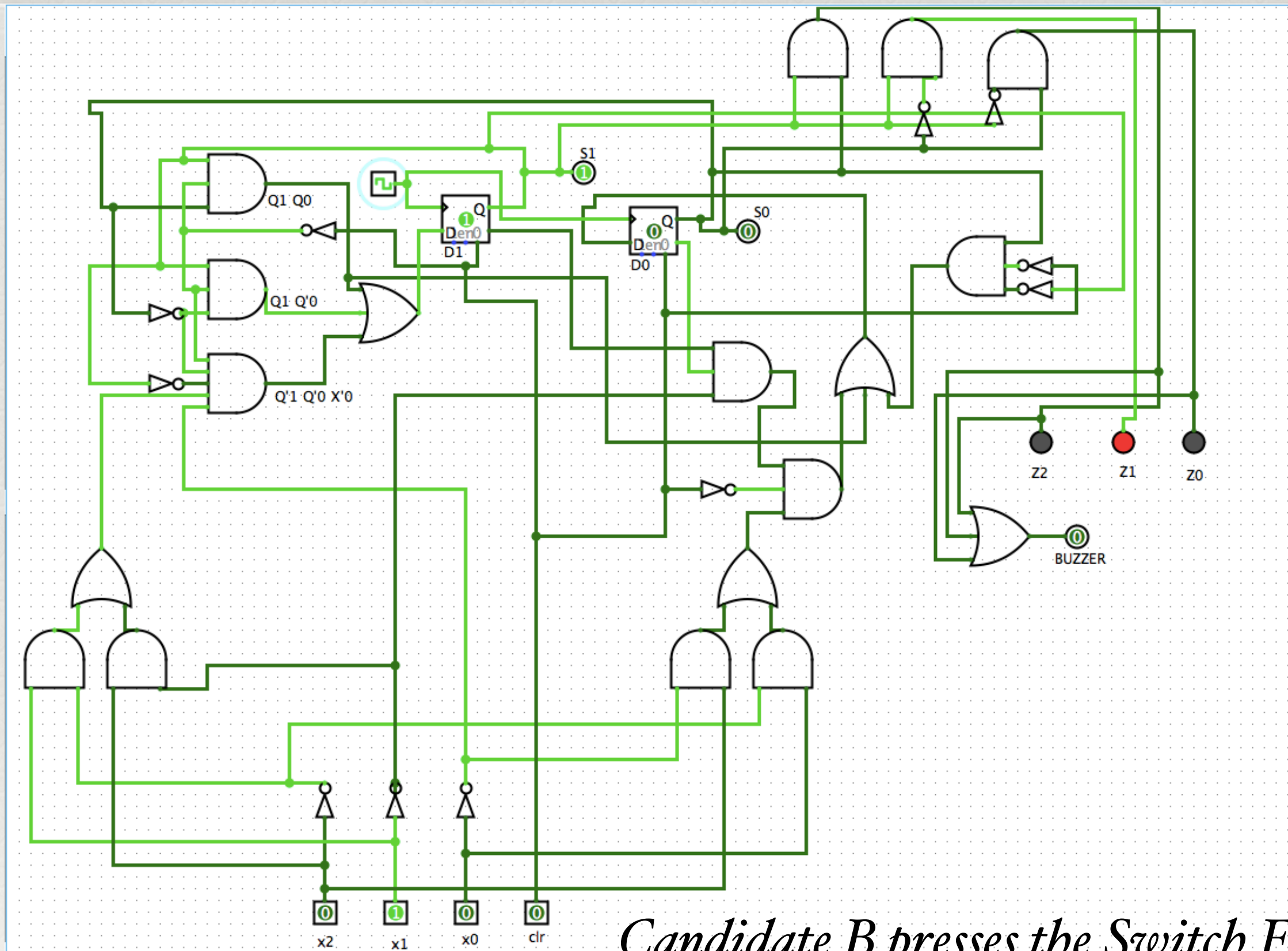


Candidate B presses the Switch First.

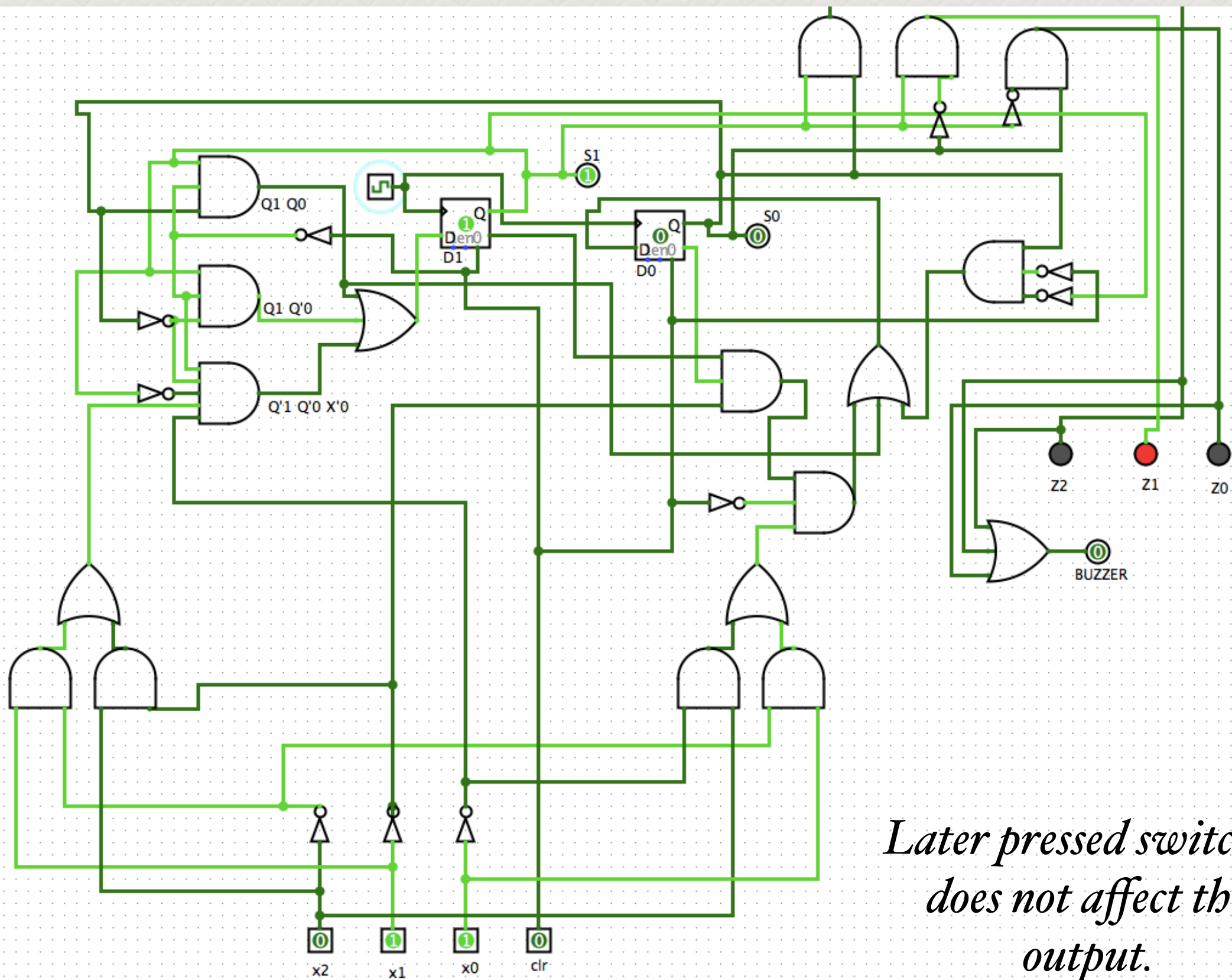

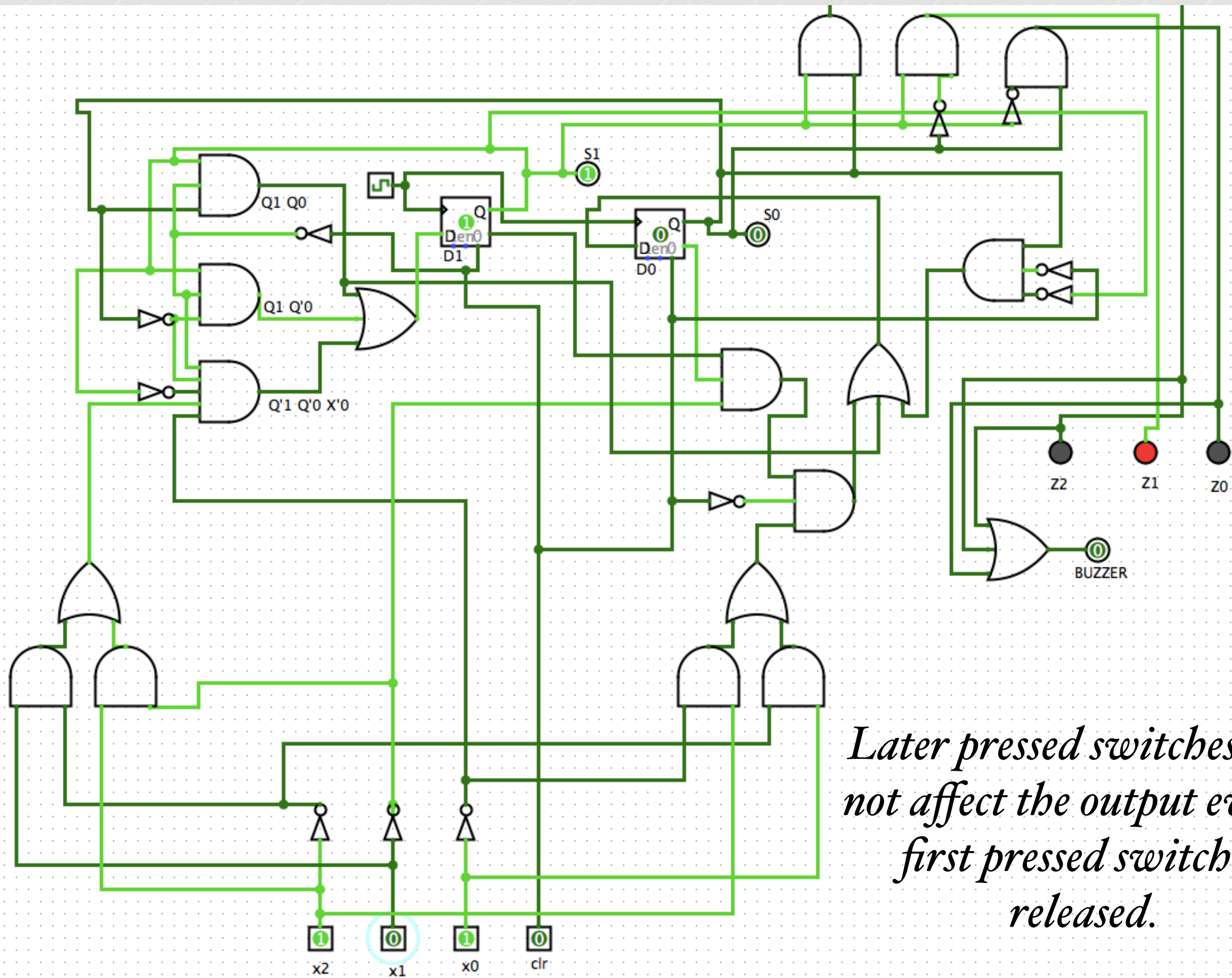*Later pressed switches
does not affect the
output.*



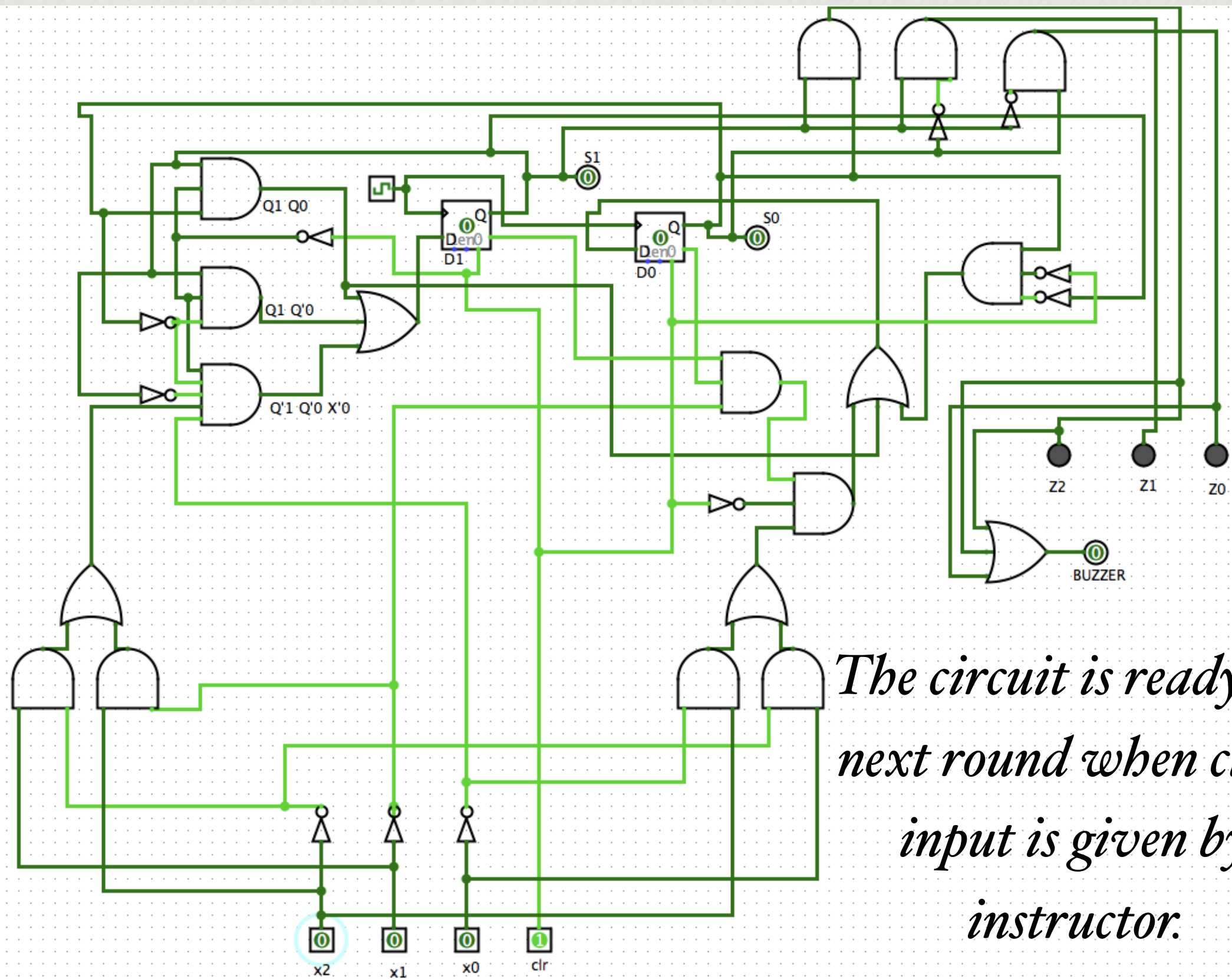Later pressed switches does not affect the output even if first pressed switch is released.



The circuit is ready for next round when clear input is given by instructor.